

# EE 5811 : FPGA LAB

## ASSIGNMENT 1

ANNU (EE21RESCH01010)

Download the codes from

<https://github.com/annu100/FPGA-LAB/tree/main/Assignment1>

### 1 PROBLEM STATEMENT-ICSE 2017-5(A)

A school intends to select candidates for an inter-School Essay competition as per the criteria given below:

- The student has participated in an earlier competition and is very creative.
- OR
- The student is very creative and has excellent awareness, but has not participated in any competition earlier.
- OR
- The student has excellent general awareness and has won prize in an inter house competition.

The inputs are

- **A:** Participated in a competition earlier.
- **B:** is very creative.
- **C:** Won prize in an inter house competition.
- **D:** has excellent general awareness.

In all the above cases, 1 indicates YES and 0 indicates NO.

**OUTPUT:** X [1 indicates YES and 0 indicates NO].

**Draw the truth table for the inputs and outputs given above and write POS expressions for it**

### 2 SOLUTION

From the truth table 2.1, maxterms are:-

$$X(A, B, C, D) = \prod (0, 1, 2, 4, 6, 7, 8, 9, 10, 11, 13, 14, 15) \quad (1)$$

Using K-Map 2.1, simplified POS expression is:

$$X = (A + D)(\bar{A} + B)(\bar{B} + \bar{C})(A + B + C)(A + C + \bar{D}) \quad (2)$$

A	B	C	D	X
0	0	0	0	0
0	0	0	1	0
0	0	1	0	0
0	0	1	1	1
0	1	0	0	0
0	1	0	1	1
0	1	1	0	0
0	1	1	1	0
1	0	0	0	0
1	0	0	1	0
1	0	1	0	0
1	0	1	1	0
1	1	0	0	1
1	1	0	1	0
1	1	1	0	0
1	1	1	1	0

TABLE 2.1: Truth Table

		CD			
		00	01	11	10
AB	00	0	0	1	0
	01	0	1	0	0
	11	1	0	0	0
	10	0	0	0	0

Fig. 2.1: Karnaugh-Map

### 2.1 Using Nand Logic:

$$X = (A + D)(\bar{A} + B)(\bar{B} + \bar{C})(A + B + C)(A + C + \bar{D}) \quad (3)$$

$$= (\bar{A}\bar{D})'(\bar{A}\bar{B})'(BC)'(\bar{A}\bar{B}\bar{C})'(\bar{A}\bar{C}D)' \quad (4)$$

$$(5)$$

Now we can draw the logic circuit using NAND gates as below.

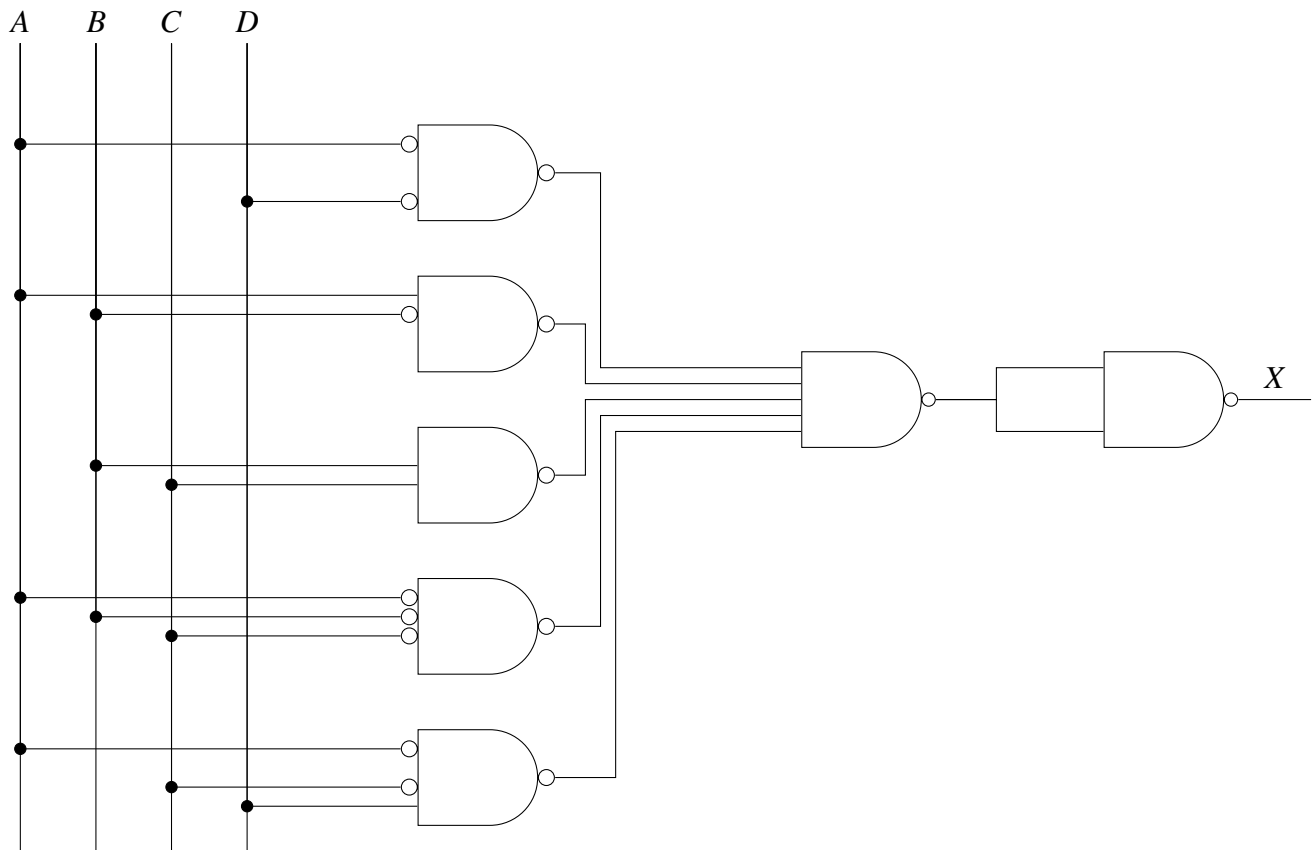


Fig. 2.2: Logic Circuit using NAND gates